

# Current Electricity

## CASE STUDY / PASSAGE BASED QUESTIONS

### Syllabus

Electric current, flow of electric charges in a metallic conductor, drift velocity, mobility and their relation with electric current; Ohm's law, electrical resistance, V-I characteristics (linear and non-linear), electrical energy and power, electrical resistivity and conductivity; temperature dependence of resistance.

Internal resistance of a cell, potential difference and emf of a cell, combination of cells in series and in parallel, Kirchhoff's laws and simple applications, Wheatstone bridge, metre bridge (qualitative ideas only)

Potentiometer - principle and its applications to measure potential difference and for comparing EMF of two cells; measurement of internal resistance of a cell (qualitative ideas only)

Questions 1-10 are Case Study based questions and are compulsory. Attempt any 4 sub parts from each question. Each question carries 1 mark.


1

### Electric Current and Current Density

The flow of charge in a particular direction constitutes the electric current. Current is measured in Ampere. Quantitatively, electric current in a conductor across an area held perpendicular to the direction of flow of charge is defined as the amount of charge is flowing across that area per unit time.

Current density at a point in a conductor is the ratio of the current at that point in the conductor to the area of cross section of the conductor of that point.

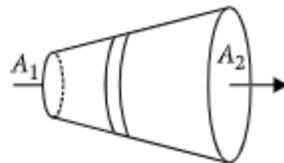The given figure shows a steady current flows in a metallic conductor of non uniform cross section. Current density depends inversely on area, so, here  $J_1 > J_2$ , as  $A_1 < A_2$ .



- (i) What is the current flowing through a conductor, if one million electrons are crossing in one millisecond through a cross-section of it ?
- (a)  $2.5 \times 10^{-10}$  A                      (b)  $1.6 \times 10^{-10}$  A  
(c)  $7.5 \times 10^{-9}$  A                      (d)  $8.2 \times 10^{-11}$  A


- (ii) SI unit of electric current is
- (a) C s                      (b) N s<sup>-2</sup>                      (c) C s<sup>-1</sup>                      (d) C<sup>-1</sup> s<sup>-1</sup>

- (iii) A steady current flows in a metallic conductor of non-uniform cross-section. Which of these quantities is constant along the conductor?

(a) Electric field    (b) Drift velocity    (c) Current                      (d) Current density

- (iv) A constant current  $I$  is flowing along the length of a conductor of variable cross-section as shown in the figure. The quantity which does not depend upon the area of cross-section is

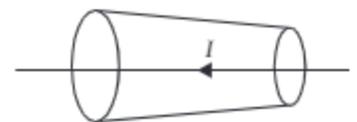(a) electron density                      (b) current density  
(c) drift velocity                      (d) electric field



- (v) When a current of 40 A flows through a conductor of area  $10 \text{ m}^2$ , then the current density is  
 (a)  $4 \text{ A/m}^2$  (b)  $1 \text{ A/m}^2$  (c)  $2 \text{ A/m}^2$  (d)  $8 \text{ A/m}^2$

2

## Factors Affecting Resistance

According to Ohm's law, the current flowing through a conductor is directly proportional to the potential difference across the ends of the conductor *i.e.*,  $I \propto V \Rightarrow \frac{V}{I} = R$ , where  $R$  is resistance of the conductor.

Electrical resistance of a conductor is the obstruction posed by the conductor to the flow of electric current through it. It depends upon length, area of cross-section, nature of material and temperature of the conductor.

We can write,  $R \propto \frac{l}{A}$  or  $R = \rho \frac{l}{A}$ , where  $\rho$  is electrical resistivity of the material of the conductor.

- (i) Dimensions of electric resistance is  
 (a)  $[\text{ML}^2\text{T}^{-2}\text{A}^{-2}]$  (b)  $[\text{ML}^2\text{T}^{-3}\text{A}^{-2}]$  (c)  $[\text{M}^{-1}\text{L}^{-2}\text{T}^{-1}\text{A}]$  (d)  $[\text{M}^{-1}\text{L}^2\text{T}^2\text{A}^{-1}]$
- (ii) If  $1 \mu\text{A}$  current flows through a conductor when potential difference of 2 volt is applied across its ends, then the resistance of the conductor is  
 (a)  $2 \times 10^6 \Omega$  (b)  $3 \times 10^5 \Omega$  (c)  $1.5 \times 10^5 \Omega$  (d)  $5 \times 10^7 \Omega$
- (iii) Specific resistance of a wire depends upon  
 (a) length (b) cross-sectional area (c) mass (d) none of these
- (iv) The slope of the graph between potential difference and current through a conductor is  
 (a) a straight line (b) curve  
 (c) first curve then straight line (d) first straight line then curve
- (v) The resistivity of the material of a wire 1.0 m long, 0.4 mm in diameter and having a resistance of 2.0 ohm is  
 (a)  $1.57 \times 10^{-6} \Omega \text{ m}$  (b)  $5.25 \times 10^{-7} \Omega \text{ m}$  (c)  $7.12 \times 10^{-5} \Omega \text{ m}$  (d)  $2.55 \times 10^{-7} \Omega \text{ m}$

3

## Temperature Dependence of Resistivity

The resistance of a conductor at temperature  $t^\circ\text{C}$  is given by  $R_t = R_0 (1 + \alpha t)$




where  $R_t$  is the resistance at  $t^\circ\text{C}$ ,  $R_0$  is the resistance at  $0^\circ\text{C}$  and  $\alpha$  is the characteristics constants of the material of the conductor.

Over a limited range of temperatures, that is not too large. The resistivity of a metallic conductor is approximately given by  $\rho_t = \rho_0(1 + \alpha t)$ .

where  $\alpha$  is the temperature coefficient of resistivity. Its unit is  $\text{K}^{-1}$  or  $^\circ\text{C}^{-1}$ .

For metals,  $\alpha$  is positive *i.e.*, resistance increases with rise in temperature.

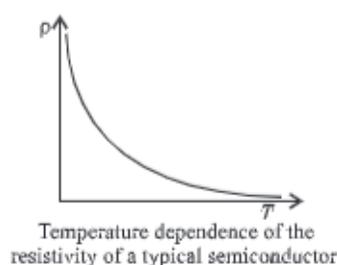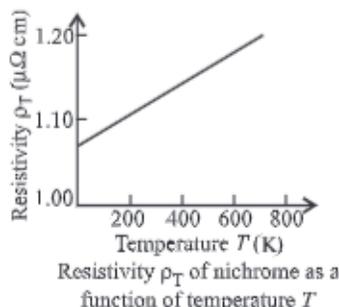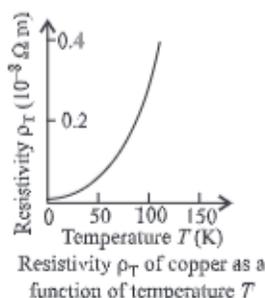For insulators and semiconductors,  $\alpha$  is negative *i.e.*, resistance decreases with rise in temperature.




- (i) Fractional increase in resistivity per unit increase in temperature is defined as  
 (a) resistivity (b) temperature coefficient of resistivity  
 (c) conductivity (d) drift velocity
- (ii) The material whose resistivity is insensitive to temperature is  
 (a) silicon (b) copper (c) silver (d) nichrome
- (iii) The temperature coefficient of the resistance of a wire is  $0.00125$  per  $^{\circ}\text{C}$ . At  $300\text{ K}$  its resistance is  $1\text{ ohm}$ . The resistance of wire will be  $2\text{ ohms}$  at  
 (a)  $1154\text{ K}$  (b)  $1100\text{ K}$  (c)  $1400\text{ K}$  (d)  $1127\text{ K}$
- (iv) The temperature coefficient of resistance of an alloy used for making resistors is  
 (a) small and positive (b) small and negative (c) large and positive (d) large and negative
- (v) For a metallic wire, the ratio  $V/I$  ( $V =$  applied potential difference and  $I =$  current flowing) is  
 (a) independent of temperature  
 (b) increases as the temperature rises  
 (c) decreases as the temperature rises  
 (d) increases or decreases as temperature rises depending upon the metal

#### 4
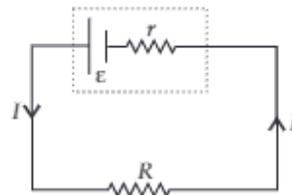
### Relation between $V$ , $\epsilon$ and $r$ of a Cell

Emf of a cell is the maximum potential difference between two electrodes of the cell when no current is drawn from the cell. Internal resistance is the resistance offered by the electrolyte of a cell when the electric current flows through it. The internal resistance of a cell depends upon the following factors; (i) distance between the electrodes (ii) nature and temperature of the electrolyte (iii) nature of electrodes (iv) area of electrodes.

For a freshly prepared cell, the value of internal resistance is generally low and goes on increasing as the cell is put to more and more use. The potential difference between the two electrodes of a cell in a closed circuit is called terminal potential difference and its value is always less than the emf of the cell in a closed circuit. It can be written as  $V = \epsilon - Ir$ .



- (i) The terminal potential difference of two electrodes of a cell is equal to emf of the cell when  
 (a)  $I \neq 0$  (b)  $I = 0$  (c) both (a) and (b) (d) neither (a) nor (b)
- (ii) A cell of emf  $\epsilon$  and internal resistance  $r$  gives a current of  $0.5\text{ A}$  with an external resistance of  $12\ \Omega$  and a current of  $0.25\text{ A}$  with an external resistance of  $25\ \Omega$ . What is the value of internal resistance of the cell?  
 (a)  $5\ \Omega$  (b)  $1\ \Omega$  (c)  $7\ \Omega$  (d)  $3\ \Omega$
- (iii) Choose the wrong statement.  
 (a) Potential difference across the terminals of a cell in a closed circuit is always less than its emf.  
 (b) Internal resistance of a cell decrease with the decrease in temperature of the electrolyte.  
 (c) Potential difference versus current graph for a cell is a straight line with a  $-ve$  slope.  
 (d) Terminal potential difference of the cell when it is being charged is given as  $V = \epsilon + Ir$ .
- (iv) An external resistance  $R$  is connected to a cell of internal resistance  $r$ , the maximum current flows in the external resistance, when  
 (a)  $R = r$  (b)  $R < r$  (c)  $R > r$  (d)  $R = 1/r$


(v) If external resistance connected to a cell has been increased to 5 times, the potential difference across the terminals of the cell increases from 10 V to 30 V. Then, the emf of the cell is

- (a) 30 V                      (b) 60 V                      (c) 50 V                      (d) 40 V

5
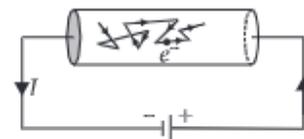
### Mechanism of Current Flow in a Conductor

Metals have a large number of free electrons nearly  $10^{28}$  per cubic metre. In the absence of electric field, average terminal speed of the electrons in random motion at room temperature is of the order of  $10^5 \text{ m s}^{-1}$ . When a potential difference  $V$  is applied across the two ends of a given conductor, the free electrons in the conductor experiences a force and are accelerated towards the positive end of the conductor. On their way, they suffer frequent collisions with the ions/atoms of the conductor and lose their gained kinetic energy. After each collision, the free electrons are again accelerated due to electric field, towards the positive end of the conductor and lose their gained kinetic energy in the next collision with the ions/atoms of the conductor. The average speed of the free electrons with which they drift towards the positive end of the conductor under the effect of applied electric field is called drift speed of the electrons.




- (i) Magnitude of drift velocity per unit electric field is
- (a) current density              (b) current                      (c) resistivity                      (d) mobility
- (ii) The drift speed of the electrons depends on
- (a) dimensions of the conductor  
(b) number density of free electrons in the conductor  
(c) both (a) and (b)  
(d) neither (a) nor (b)
- (iii) We are able to obtain fairly large currents in a conductor because
- (a) the electron drift speed is usually very large  
(b) the number density of free electrons is very high and this can compensate for the low values of the electron drift speed and the very small magnitude of the electron charge  
(c) the number density of free electrons as well as the electron drift speeds are very large and these compensate for the very small magnitude of the electron charge  
(d) the very small magnitude of the electron charge has to be divided by the still smaller product of the number density and drift speed to get the electric current.
- (iv) Drift speed of electrons in a conductor is very small *i.e.*,  $i = 10^{-4} \text{ m s}^{-1}$ . The Electric bulb glows immediately. When the switch is closed because
- (a) drift velocity of electron increases when switch is closed  
(b) electrons are accelerated towards the negative end of the conductor  
(c) the drifting of electrons takes place at the entire length of the conductor  
(d) the electrons of conductor move towards the positive end and protons of conductor move towards negative end of the conductor.
- (v) The number density of free electrons in a copper conductor is  $8.5 \times 10^{28} \text{ m}^{-3}$ . How long does an electron take to drift from one end of a wire 3.0 m long to its other end? The area of cross-section of the wire is  $2.0 \times 10^{-6} \text{ m}^2$  and it is carrying a current of 3.0 A.
- (a)  $8.1 \times 10^4 \text{ s}$                       (b)  $2.7 \times 10^4 \text{ s}$                       (c)  $9 \times 10^3 \text{ s}$                       (d)  $3 \times 10^3 \text{ s}$
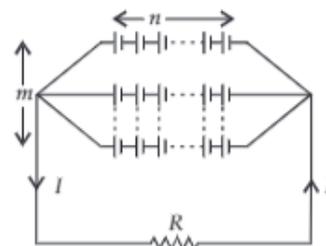
## Grouping of Cells

A single cell provides a feeble current. In order to get a higher current in a circuit, we often use a combination of cells. A combination of cells is called a battery. Cells can be joined in series, parallel or in a mixed way.

Two cells are said to be connected in series when negative terminal of one cell is connected to positive terminal of the other cell and so on. Two cells are said to be connected in parallel if positive terminal of each cell is connected to one point and negative terminal of each cell connected to the other point. In mixed grouping of cells, a certain number of identical cells are joined in series, and all such rows are then connected in parallel with each other.




- (i) To draw the maximum current from a combination of cells, how should the cells be grouped?
- Parallel
  - Series
  - Mixed grouping
  - Depends upon the relative values of internal and external resistances
- (ii) The total emf of the cells when  $n$  identical cells each of emf  $\epsilon$  are connected in parallel is
- $n\epsilon$
  - $n^2\epsilon$
  - $\epsilon$
  - $\frac{\epsilon}{n}$
- (iii) 4 cells each of emf 2 V and internal resistance of  $1 \Omega$  are connected in parallel to a load resistor of  $2 \Omega$ . Then the current through the load resistor is
- 2 A
  - 1.5 A
  - 1 A
  - 0.888 A
- (iv) If two cells out of  $n$  number of cells each of internal resistance ' $r$ ' are wrongly connected in series, then total resistance of the cell is
- $2nr$
  - $nr - 4r$
  - $nr$
  - $r$
- (v) Two identical non-ideal batteries are connected in parallel. Consider the following statements.
- The equivalent emf is smaller than either of the two emfs.
  - The equivalent internal resistance is smaller than either of the two internal resistances.
- Both (i) and (ii) are correct.
  - (i) is correct but (ii) is wrong.
  - (ii) is correct but (i) is wrong.
  - Both (i) and (ii) are wrong.

## Kirchhoff's Rules

In 1942, a German physicist Kirchhoff extended Ohm's law to complicated circuits and gave two laws, which enable us to determine current in any part of such a circuit.

According to Kirchhoff's first rule, the algebraic sum of the currents meeting at a junction in a closed electric circuit is zero. The current flowing in a conductor towards the junction is taken as positive and the current flowing away from the junction is taken as negative.

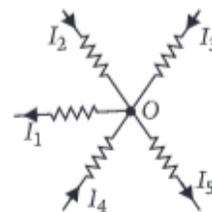
According to Kirchhoff's second rule, in a closed loop, the algebraic sum of the emf's and algebraic sum of the products of current and resistance in the various arms of the loop is zero. While traversing a loop, if negative pole of the cell is encountered first, then its emf is negative, otherwise positive.



- (i) Kirchoff's I<sup>st</sup> law follows
- (a) law of conservation of energy  
(b) law of conservation of charge  
(c) law of conservation of momentum  
(d) Newton's third law of motion
- (ii) The value of current  $I$  in the given circuit is
- (a) 4.5 A  
(b) 3.7 A  
(c) 2.0 A  
(d) 2.5 A
- (iii) Kirchoff's II<sup>nd</sup> law is based on.
- (a) law of conservation of momentum of electron  
(b) law of conservation of charge and energy  
(c) law of conservation of energy  
(d) none of these.



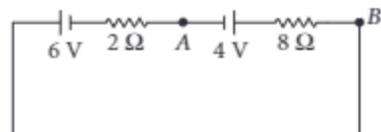- (iv) Point out the right statements about the validity of Kirchoff's Junction rule.
- (a) The current flowing towards the junction are taken as positive.  
(b) The currents flowing away from the junction are taken as negative.  
(c) bending or reorienting the wire does not change the validity of Kirchoff's Junction rule.  
(d) All of the above
- (v) Potential difference between  $A$  and  $B$  in the circuit shown here is
- (a) 4 V  
(b) 5.6 V  
(c) 2.8 V  
(d) 6 V



## 8

### Wheatstone Bridge and its Applications


Wheatstone bridge is an arrangement of four resistances  $P$ ,  $Q$ ,  $R$  and  $S$  connected as shown in the figure. Their values are so adjusted that the galvanometer  $G$  shows no deflection. The bridge is then said to be balanced when this condition is achieved happens. In the setup shown here, the points  $B$  and  $D$  are at the same potential and

it can be shown that  $\frac{P}{Q} = \frac{R}{S}$

This is called the balancing condition. If any three resistances are known, the fourth can be found.

The practical form of Wheatstone bridge is slide wire bridge or Meter bridge. Using this the unknown resistance

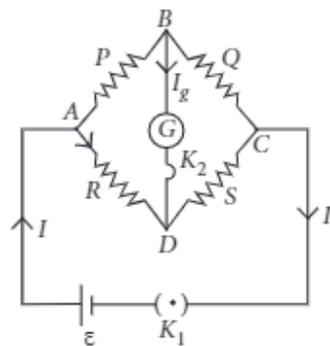can be determined as  $S = \left(\frac{100-l}{l}\right) \times R$ , where  $l$  is the balancing length of the Meter bridge.




- (i) In a Wheatstone bridge circuit,  $P = 5 \Omega$ ,  $Q = 6 \Omega$ ,  $R = 10 \Omega$  and  $S = 5 \Omega$ . What is the value of additional resistance to be used in series with  $S$ , so that the bridge is balanced?
- (a)  $9 \Omega$                       (b)  $7 \Omega$                       (c)  $10 \Omega$                       (d)  $5 \Omega$
- (ii) A Wheatstone bridge consisting of four arms of resistances  $P$ ,  $Q$ ,  $R$ ,  $S$  is most sensitive when
- (a) all the resistances are equal  
(b) all the resistances are unequal  
(c) the resistances  $P$  and  $Q$  are equal but  $R \gg P$  and  $S \gg Q$   
(d) the resistances  $P$  and  $Q$  are equal but  $R \ll P$  and  $S \ll Q$ .

- (iii) When a metal conductor connected to left gap of a meter bridge is heated, the balancing point  
 (a) shifts towards right (b) shifts towards left (c) remains unchanged (d) remains at zero.
- (iv) The percentage error in measuring resistance with a meter bridge can be minimized by adjusting the balancing point close to  
 (a) 0 (b) 20 cm (c) 50 cm (d) 80 cm
- (v) In a meter bridge experiment, the ratio of left gap resistance to right gap resistance is 2 : 3. The balance point from left is  
 (a) 20 cm (b) 50 cm (c) 40 cm (d) 60 cm

9
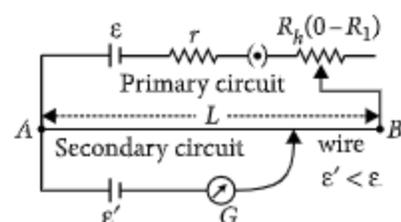
## Potentiometer : An Ideal Voltmeter


Potentiometer is an apparatus used for measuring the emf of a cell or potential difference between two points in an electrical circuit accurately. It is also used to determine the internal resistance of a primary cell. The potentiometer is based on the principle that, if  $V$  is the potential difference across any portion of the wire of length  $l$  and resistance  $R$ , then  $V \propto l$  or  $V = kl$  where  $k$  is the potential gradient. Thus, potential difference across any portion of potentiometer wire is directly proportional to length of the wire of that portion. The potentiometer wire must be uniform. The resistance of potentiometer wire should be high.



- (i) Which one of the following is true about potentiometer?  
 (a) Its sensitivity is low.  
 (b) It measures the emf of a cell very accurately.  
 (c) It is based on deflection method.
- (ii) A current of 1.0 mA is flowing through a potentiometer wire of length 4 cm and of resistance 4  $\Omega$ . The potential gradient of the potentiometer wire is  
 (a)  $10^{-3}$  V m $^{-1}$  (b)  $10^{-5}$  V m $^{-2}$  (c)  $2 \times 10^{-3}$  V m $^{-1}$  (d)  $4 \times 10^{-3}$  V m $^{-1}$
- (iii) Sensitivity of a potentiometer can be increased by  
 (a) decreasing potential gradient along the wire (b) increasing potential gradient along the wire  
 (c) decreasing current through the wire (d) increasing current through the wire
- (iv) A potentiometer is an accurate and versatile device to make electrical measurements of EMF because the method involves  
 (a) potential gradients  
 (b) a condition of no current flow through the galvanometer  
 (c) a combination of cells, galvanometer and resistances  
 (d) cells
- (v) In a potentiometer experiment, the balancing length is 8 m, when the two cells  $E_1$  and  $E_2$  are joined in series. When the two cells are connected in opposition the balancing length is 4 m. The ratio of the e. m. f. of two cells ( $E_1/E_2$ ) is  
 (a) 1 : 2 (b) 2 : 1 (c) 1 : 3 (d) 3 : 1
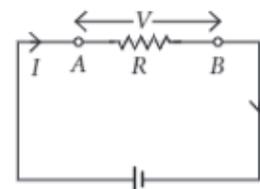
## Heat produced by Electric Current

Whenever an electric current is passed through a conductor, it becomes hot after some time. The phenomenon of the production of heat in a resistor by the flow of an electric current through it is called heating effect of current or Joule heating. Thus, the electrical energy supplied by the source of emf is converted into heat. In purely resistive circuit, the energy expended by the source entirely appears as heat. But if the circuit has an active element like a motor, then a part of the energy supplied by the source goes to do useful work and the rest appears as heat. Joule's law of heating form the basis of various electrical appliances such as electric bulb, electric furnace, electric press etc.



- (i) Which of the following is a correct statement?
- Heat produced in a conductor is independent of the current flowing.
  - Heat produced in a conductor varies inversely as the current flowing.
  - Heat produced in a conductor varies directly as the square of the current flowing.
  - Heat produced in a conductor varies inversely as the square of the current flowing.
- (ii) If the coil of a heater is cut to half, what would happen to heat produced ?
- Doubled
  - Halved
  - Remains same
  - Becomes four times
- (iii) A 25 W and 100 W are joined in series and connected to the mains. Which bulbs will glow brighter ?
- 100 W
  - 25 W
  - both bulbs will glow brighter
  - none will glow brighter
- (iv) A rigid container with thermally insulated wall contains a coil of resistance  $100 \Omega$ , carrying current 1 A. Change in its internal energy after 5 min will be
- 0 kJ
  - 10 kJ
  - 20 kJ
  - 30 kJ
- (v) The heat emitted by a bulb of 100 W in 1 min is
- 100 J
  - 1000 J
  - 600 J
  - 6000 J

## ASSERTION & REASON

For question numbers 11-30, two statements are given-one labelled Assertion (A) and the other labelled Reason (R). Select the correct answer to these questions from the codes (a), (b), (c) and (d) as given below.

- Both A and R are true and R is the correct explanation of A
- Both A and R are true but R is NOT the correct explanation of A
- A is true but R is false
- A is false and R is also false

11. **Assertion :** Current is a scalar quantity.

**Reason :** Electric current arises due to continuous flow of charged particles or ions.

12. **Assertion :** Insulator do not allow flow of current through them.

**Reason :** Insulator have no free charge carrier.

13. **Assertion :** The drift velocity of electrons in a metallic wire will decrease, if the temperature of the wire is increased.  
**Reason :** On increasing temperature, conductance of metallic wire decreases.
14. **Assertion :** The current flowing through a conductor is directly proportional to the drift velocity.  
**Reason :** As the drift velocity increases the current following through the conductor decreases.
15. **Assertion :** Chemical reactions involved in primary cells are irreversible and in secondary cells are reversible.  
**Reason :** Primary cells can be recharged, but secondary cells can not be recharged.
16. **Assertion :** The average thermal velocity of the electrons in a conductor is zero.  
**Reason :** Direction of motion of electrons are randomly oriented.
17. **Assertion :** If the length of the conductor is doubled, the drift velocity will become half of the original value (keeping potential difference unchanged).  
**Reason :** At constant potential difference, drift velocity is inversely proportional to the length of the conductor.
18. **Assertion :** The temperature coefficient of resistance is always positive only for metals.  
**Reason :** On increasing the temperature, the resistance of metals and alloys increases.
19. **Assertion :** Material used in the construction of a standard resistance is constantan or manganin.  
**Reason :** Temperature coefficient of constantan is very small.
20. **Assertion :** kWhr is a commercial unit used for expressing consumed electric energy.  
**Reason :** Kilo-watt hour is the unit of electric power.
21. **Assertion :** The 200 W bulbs glows with more brightness than 100 W bulbs.  
**Reason :** A 100 watt bulb has more resistance than a 200 W bulb.
22. **Assertion :** Heater wire must have high resistance and high melting point.  
**Reason :** If resistance is high, the electric conductivity will be less.
23. **Assertion :** Fuse wire must have high resistance and low melting point.  
**Reason :** Fuse is used for small current flow only.
24. **Assertion :** In a chain of bulbs, 50 bulbs are joined in series. One bulb is removed now the circuit is again completed. If the remaining 49 bulbs are again connected in series across the same supply, then light gets decreased in the room.  
**Reason :** The resistance of 49 bulbs will be more than 50 bulbs.
25. **Assertion :** Two electric bulbs of 50 and 100 watt are given. When connected in series 50 watt bulb glows more but when connected in parallel 100 watt bulb glows more.  
**Reason :** In series combination, power is directly proportional to the resistance of circuit. But in parallel combination, power is inversely proportional to the resistance of the circuit.
26. **Assertion :** Two bulbs of same wattage, one having a carbon filament and the other having a metallic filament are connected in series. Metallic bulbs will glow more brightly than carbon filament bulb.  
**Reason :** Carbon is a semiconductor.
27. **Assertion :** It is advantageous to transmit electric power at high voltage.  
**Reason :** High voltage implies high current.
28. **Assertion :** A person touching a high power line gets stuck with the line.  
**Reason :** The current carrying wire attracts the man towards it.
29. **Assertion :** Though the same current flows through the live wires and the filament of the bulb but heat produced in the filament is much higher than that in live wires.  
**Reason :** The filament of bulbs is made of a material of high resistance and high melting point.
30. **Assertion :** The current in a wire is due to flow of free electrons in a definite direction.  
**Reason :** A current carrying wire should have non-zero charge.

## HINTS & EXPLANATIONS

1. (i) (b):  $q = 10^6 \times 1.6 \times 10^{-19} \text{ C} = 1.6 \times 10^{-13} \text{ C}$   
 $t = 10^{-3} \text{ s}$

$$I = \frac{q}{t} = \frac{1.6 \times 10^{-13}}{10^{-3}} = 1.6 \times 10^{-10} \text{ A}$$

(ii) (c):  $\text{C s}^{-1}$

(iii) (c): The current flowing through a conductor of non-uniform cross-section remain same in the whole of the conductor.

(iv) (a): When a constant current is flowing through a conductor of non-uniform cross-section, electron density does not depend upon the area of cross section, while current density, drift velocity and electric field all vary inversely with area of cross-section.

(v) (a): Given,  $I = 40 \text{ A}$ ;  $A = 10 \text{ m}^2$

$\therefore$  Current density,  $J = \frac{I}{A}$  or  $J = \frac{40}{10} = 4 \text{ A/m}^2$

2. (i) (b)

(ii) (a):  $R = \frac{V}{I} = \frac{2}{10^{-6}} = 2 \times 10^6 \Omega$

(iii) (d): Specific resistance depends upon the nature of material and is independent of mass and dimensions of the material.

(iv) (a)

(v) (d):  $l = 1.0 \text{ m}$ ;  $D = 0.4 \text{ mm} = 4 \times 10^{-4} \text{ m}$   
 $R = 2 \Omega$

$$A = \frac{\pi D^2}{4} = \frac{\pi \times (4 \times 10^{-4})^2}{4} = 4\pi \times 10^{-8} \text{ m}^2$$

Now,  $\rho = \frac{RA}{l} = \frac{2 \times 4\pi \times 10^{-8}}{1} = 2.55 \times 10^{-7} \Omega \text{ m}$

3. (i) (b): Temperature coefficient of resistivity is defined as the fractional increase in resistivity per unit increase in temperature.

(ii) (d): Nichrome (which is an alloy of nickel, iron and chromium) exhibits a very weak dependence of resistivity with temperature.

(iii) (d): Using,  $R_T = R_0(1 + \alpha T)$

$$\therefore \frac{R_{T_2}}{R_{T_1}} = \frac{R_0(1 + \alpha T_2)}{R_0(1 + \alpha T_1)} = \frac{2}{1} = \frac{(1 + \alpha T_2)}{(1 + \alpha \times 300)}$$

$$\Rightarrow 2 + \alpha \times 600 = 1 + \alpha T_2$$

$$\Rightarrow 1 = \alpha (T_2 - 600) \Rightarrow \frac{1}{0.00125} = (T_2 - 600)$$

$$\Rightarrow 800^\circ\text{C} = T_2 - 600$$

$$T_2 = 800 + 273 + 600$$

$$T_2 = 1127 \text{ K}$$

(iv) (a): The temperature coefficient of resistance of an alloy used for making resistors is small and positive.

(v) (b): The resistance of a metallic wire at temperature  $t^\circ\text{C}$  is given by

$$R_t = R_0(1 + \alpha t), \text{ where } \alpha \text{ is the temperature coefficient of resistance and } R_0 \text{ is the resistance of a wire at } 0^\circ\text{C}.$$

For metals,  $\alpha$  is positive. Hence, resistance of a wire increases with increase in temperature.

Also, from Ohm's law

$$\frac{V}{I} = R$$

Hence on increasing the temperature, the ratio  $\frac{V}{I}$  increases.

4. (i) (b)

(ii) (b): As  $I = \frac{\epsilon}{R + r}$

In first case,  $I = 0.5 \text{ A}$ ;  $R = 12 \Omega$

$$0.5 = \frac{\epsilon}{12 + r} \Rightarrow \epsilon = 6.0 + 0.5r \quad \dots(i)$$

In second case,  $I = 0.25 \text{ A}$ ;  $R = 25 \Omega$

$$\epsilon = 6.25 + 0.25r \quad \dots(ii)$$

From equation (i) and (ii),  $r = 1 \Omega$

(iii) (b)

(iv) (a): Current in the circuit  $I = \frac{E}{R + r}$

Power delivered to the resistance  $R$  is

$$P = I^2 R = \frac{E^2 R}{(R + r)^2}$$

It is maximum when  $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = E^2 \left[ \frac{(r + R)^2 - 2R(r + R)}{(r + R)^4} \right] = 0$$

or  $(r + R)^2 = 2R(r + R)$  or  $R = r$

(v) (b): For first case,  $\frac{\epsilon}{R + r} = \frac{10}{R} \quad \dots(i)$

For second case,  $\frac{\epsilon}{5R+r} = \frac{30}{5R}$  ... (ii)

Dividing (i) by (ii), we get  $r = 5R$

From (i),  $\frac{E}{R+5R} = \frac{10}{R}$

$E = 60 \text{ V}$

5. (i) (d): Mobility is defined as the magnitude of drift velocity per unit electric field.

Mobility,  $\mu = \frac{|v_d|}{E}$

(ii) (c): Drift velocity,  $v_d = \frac{I}{neA}$

where the symbols have their usual meanings.

(iii) (b):  $I = neAv_d$

$v_d$  is of order of few  $\text{m s}^{-1}$ ,  $e = 1.6 \times 10^{-19} \text{ C}$ ,

$A$  is of the order of  $\text{mm}^2$ , so a large  $I$  is due to a large value of  $n$  in conductors.

(iv) (c): When we close the circuit, an electric field is established instantly with the speed of electromagnetic wave which causes electrons to drift at every portion of the circuit, due to which the current is set up in the entire circuit instantly. The current which is set up does not wait for electrons to flow from one end of the conductor to another. Thus, the electric bulb glows immediately when switch is closed.

(v) (b): Here,

Number density of free electrons,  $n = 8.5 \times 10^{28} \text{ m}^{-3}$

Area of cross-section of a wire,  $A = 2.0 \times 10^{-6} \text{ m}^2$

Length of the wire,  $l = 3.0 \text{ m}$

Current,  $I = 3.0 \text{ A}$

The drift velocity of an electron is

$v_d = \frac{I}{neA}$  ... (i)

The time taken by the electron to drift from one end to other end of the wire is

$t = \frac{l}{v_d} = \frac{lneA}{I}$  (Using (i))

$= \frac{(3.0 \text{ m})(8.5 \times 10^{28} \text{ m}^{-3})(1.6 \times 10^{-19} \text{ C})(2.0 \times 10^{-6} \text{ m}^2)}{(3.0 \text{ A})}$

$= 2.7 \times 10^4 \text{ s}$

6. (i) (d)

(ii) (c): For parallel combination of  $n$  cells,  $\epsilon_{eq} = \epsilon$ .


(iii) (d):  $I = \frac{mE}{mR+r}$ ,  $m = \text{number of cells} = 4$

$E = 2 \text{ V}$ ,  $R = 2 \Omega$ ,  $r = 1 \Omega$

$I = \frac{8}{8+1} = \frac{8}{9} = 0.888 \text{ A}$

(iv) (b)

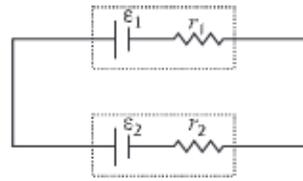(v) (c): Let two cells of emf's  $\epsilon_1$  and  $\epsilon_2$  and of internal resistance  $r_1$  and  $r_2$  respectively are connected in parallel.



The equivalent emf is given by

$\epsilon_{eq} = \frac{\epsilon_1 r_2 + \epsilon_2 r_1}{r_1 + r_2}$  ... (i)

The equivalent internal resistance is given by

$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2}$  or  $r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$  ... (ii)

Let us consider, two cells connected in parallel of same emf  $\epsilon$  and same internal resistance  $r$ .


From equation (i), we get  $\epsilon_{eq} = \frac{\epsilon r + \epsilon r}{r + r} = \epsilon$

From equation (ii), we get

$r_{eq} = \frac{r^2}{r + r} = \frac{r}{2}$

7. (i) (a): Kirchhoff's I<sup>st</sup> law is based on law of conservation of charge whereas Kirchhoff's II<sup>nd</sup> law is based on law of conservation of energy.

(ii) (c):

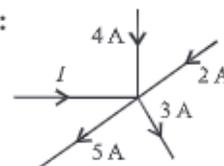

According to Kirchhoff's junction law


$(+I) + (+4 \text{ A}) + (+2 \text{ A}) + (-5 \text{ A}) + (-3 \text{ A}) = 0$

$I + 6 \text{ A} - 8 \text{ A} = 0$  or  $I = 2 \text{ A}$

(iii) (c)

(iv) (d)

(v) (b):

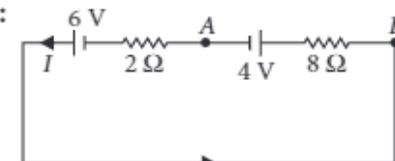

Apply KVL in the given circuit,

$6 - 8I - 4 - 2I = 0$

or,  $2 - 10I = 0$ , or,  $I = 2/10 = 0.2 \text{ A}$

$V_{AB} = 4 + I \times 8 = 4 + 0.2 \times 8 = 5.6 \text{ V}$


8. (i) (b):  $(S + x) = \frac{Q}{P} R$

$$x = \frac{Q}{P} R - S = \frac{6}{5} \times 10 - 5 = 7 \Omega$$

(ii) (a): A Wheatstone bridge consisting of four arms of resistance  $P, Q, R, S$  is most sensitive when all the resistances are equal.

(iii) (a): When metal wire is heated, its resistance increases.  $R_1$  increases,  $l_1$  increases.

The null point shift to the right.

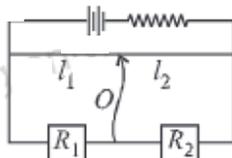

(iv) (c): The percentage error in measuring resistance with a metre bridge can be minimized by adjusting the balancing point near the middle of the bridge *i.e.* close to 50 cm.

(v) (c):  $\frac{P}{Q} = \frac{l_1}{100 - l_1}$  or  $\frac{2}{3} = \frac{l_1}{100 - l_1}$

or  $5l_1 = 200$  or  $l_1 = 40$  cm

9. (i) (b)

(ii) (a): Given,  $I = 1.0$  mA =  $10^{-3}$  A;  $R = 4 \Omega$ ;  $L = 4$  m

Potential drop across potentiometer wire,

$$V = IR = 10^{-3} \times 4 \text{ V}$$

Potential gradient,  $k = \frac{V}{L} = \frac{4 \times 10^{-3}}{4}$   
 $= 10^{-3} \text{ V m}^{-1}$

(iii) (a)

(iv) (b): A potentiometer is an accurate and versatile device to make electrical measurements of EMF because the method involves a condition of no current flow through the galvanometer. It can be used to measure potential difference, internal resistance of a cell and compare EMF's of two sources.

(v) (d):  $\frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2} = \frac{8 + 4}{8 - 4} = \frac{12}{4} = \frac{3}{1}$

10. (i) (c): According to Joule's law of heating,

Heat produced in a conductor,  $H = I^2 R t$

where,  $I$  = Current flowing through the conductor

$R$  = Resistance of the conductor

$t$  = Time for which current flows through the conductor.

$\therefore H \propto I^2$

(ii) (a): If the coil is cut into half, its resistance is also halved.

As  $H = \frac{V^2}{R} t \therefore H' = 2$

(iii) (b):  $P = \frac{V^2}{R}$  or  $R = \frac{V^2}{P}$

The bulbs are joined in series. Current in both the bulbs will same.

$\therefore$  The heat produced in them is given by  $H = I^2 R t$

or  $H \propto R \Rightarrow H \propto \frac{1}{P}$

Therefore the bulb with low wattage or high resistance will glow brighter or we can say the 25 W bulb will glow brighter than the 100 W bulb.

(iv) (d):  $R = 100 \Omega$ ;  $I = 1$  A;  $t = 5$  min. =  $5 \times 60 = 300$  s  
 change in internal energy = heat generated in coil  
 $= I^2 R t = ((1)^2 \times 100 \times 300) \text{ J}$   
 $= 30000 \text{ J} = 30 \text{ kJ}$

(v) (d): Here,  $P = 100$  W,  $t = 1$  min = 60 s

Heat developed in time  $t$

$$H = P \times t = (100 \text{ W})(60 \text{ s}) = 6000 \text{ J}$$

11. (b): Current is a scalar quantity, it is justified by the following two observations

(i) If current carrying wire is bent at some point, then also current in the wire remains same, while a vector quantity always changes by changing its direction.

(ii) Current flowing in the circuit do not follow the laws of vector addition. It follows according to ordinary rule of algebra. This makes it clear that current is not a vector but a scalar quantity. Also current is defined as rate of flow of charge through the wire  $I = dq/dt$ .

12. (a): Since current arises due to continuous flow of charged particles. There is no free charge in insulator hence no flow of charges are possible. Therefore current do not flow through insulators.

13. (b): On increasing temperature of wire the kinetic energy of free electrons increase and so they collide more rapidly with each other and hence their drift velocity decreases. Also when temperature increases, resistance increase and resistance is inversely proportional to conductivity of material.

14. (c): Consider a conductor of length  $l$  and area of cross section  $A$ . Time taken by the free electrons to cross the conductor,  $t = l/v_d$

Hence, current,  $I = \frac{q}{t} = \frac{Al \times ne}{l/v_d}$

or,  $I = Anev_d$

or,  $I \propto v_d$

Thus current is directly proportional to drift velocity.

15. (c): Primary cells cannot be recharged because they involve irreversible reactions. Secondary cells can be recharged because they involve reversible reactions.

16. (a): In normal conductor, the direction of electrons are randomly oriented such that the total sum of their velocities is equal to zero.

17. (a): Drift velocity of free electrons is given by,

$$v_d = \frac{eE}{m} \tau$$

$$\text{where, } E = \frac{\text{Potential difference}}{\text{length}} = \frac{V}{l}$$

$$\therefore v_d = \frac{eV}{ml} \tau \text{ i.e., } v_d \propto 1/l \text{ where, } \frac{eV\tau}{m} \text{ is constant.}$$

It mean if  $l$  is doubled, the drift velocity will become half of the original value.

18. (b): The value of temperature coefficient of resistance is positive only for metals and alloys and is negative for semiconductors and insulators.

19. (a): These alloys (constantan or manganin) are used for making standard resistance because they possess high resistivity and low temperature coefficient of resistance.

$$20. (c): 1 \text{ kWhr} = 1 \text{ kW} \times 1 \text{ hour} \\ = 1000 \text{ (joule/sec)} \times 3600 \text{ sec} = 36 \times 10^5 \text{ joule}$$

i.e., kWhr is the unit of electric energy and used for expressing consumed electric energy.

$$21. (b): \text{The resistance, } R = \frac{V^2}{P}, \text{ i.e., } R \propto 1/P$$

i.e., higher is the wattage of a bulb, lesser is the resistance and so it will glow bright.

22. (b): Heater wire must have high resistance and high melting point, because in series current remains same, therefore according to Joule's law  $H = i^2 R t / 4.2$ , heat produced is high if  $R$  is high. Melting point must be high, so that wire may not melt with increase in temperature.

23. (c): Fuse wire must have high resistance because in series, current remains same. Therefore according to Joule's law  $H = \frac{i^2 R t}{4.2}$ , heat produced is high if  $R$  is high. The melting point must be low so that wire may melt with increase in temperature. As a current larger

than the specified value flows through the circuit the temperature of the fuse wire increases. This melts the fuse wire and breaks the circuit.

24. (d): Since the bulbs are joined in series, so when one bulb is removed from chain then the resistance of the chain is decreased, hence current flowing through each bulb is increased. As heat produced  $\propto i^2$ , hence light gets increased in the room.

25. (a): Resistance of 50 watt bulb is two times the resistance of 100 watt bulb. When bulbs are connected in series, 50 watt bulb will glow more as  $P = i^2 R$  (current remains same in series). In parallel, the 100 watt bulb will glow more as  $P = V^2 / R$  (potential difference remain same in parallel).

26. (d): When two bulbs are connected in series, the resistance of the circuit increases and so the voltage in each decreases, hence the brightness and the temperature also decreases. Due to decrease in temperature, the resistance of the carbon filament will slightly increase while that of metal filament will decrease. Hence, carbon filament bulb will glow more brightly ( $P = i^2 R$ ). Also carbon is not a semiconductor.

27. (c): As  $P = Vi$ , hence for the transmission of same power, high voltage implies less current. Therefore heat energy losses ( $H = i^2 R t / 4.2$ ) are minimized if power is transmitted at high voltage.

28. (d): Because there is no special attractive force

that keeps a person stuck with a high power line. The actual reason is that a current of the order of 0.05 A or even less is enough to bring disorder in our nervous system. As a result of it, the affected person may lose temporarily his ability to control his nervous system to get himself free from the high power line.

29. (b): As filament of bulb and live wire are in series, hence current through both is same. Now, because  $H = \frac{i^2 R t}{4.2}$  and resistance of the filament of the bulb is much higher than that of live wires, hence heat produced in the filament is much higher than that in line wires.

30. (c): The current in a wire is due to flow of free electrons in a definite direction. But the number of protons in the wire at any instant is equal to number of electrons and charge on electrons is equal and opposite to that of proton. Hence, net charge on the wire is zero.